#### 2022年2月28日9:40-10:40

大学院工学研究科 電気エネルギーシステム専攻

通信工学専攻

電子工学専攻

大学院情報科学研究科 情報·生命系群

大学院医工学研究科 工学系コース電気・情報系

# 大学院入学試験問題

# 基礎科目 Basic Subjects

注意: 6 設問中, 2 問題を選んで, 答案用紙(問題ごとに1枚)に解答せよ. 答案用紙が不足する場合は裏面を使って良い. 問題は和文と英文を併記してある.

**Attention:** Choose 2 questions out of the following 6 questions and answer each of them on a separate answer sheet. You may use the backside. Questions are written in both Japanese and English.

#### 2022 年 2·3 月実施 問題1 電磁気学 (1頁目/2頁中)

Fig. 1 に示すように,無損失導体からなる円形のコイルが円形電流 I の上にある.円形電流 I および円形コイルは xy 面に平行であり,それらの半径はそれぞれ a,b である.円形電流 I および円形コイルの中心はそれぞれ (x,y,z)=(0,0,0) および (x,y,z)=(0,0,h) である.円形コイルの巻数は 1 とする.円形コイルには微小の隙間があり,誘導電圧 V が励起される.円形電流 I は 閉経路 C に沿って流れている.C 上の線素ベクトルは dI とする.円形電流 I および線素ベクトルは dI の向きは Fig. 1 に示す.円形電流 I および円形コイルは真空中にある.位置ベクトルは r とする.真空の透磁率は  $\mu_0$  である.以下の間に答えよ.

- (1) ファラデーの電磁誘導の法則を示し、その物理的意味を説明せよ.
- (2) 円形電流 I の磁気双極子モーメント m は以下のように定義される。m を求めよ。

$$m = \frac{\mu_0 I}{2} \oint_C r \times dl$$

- (3) 円形コイルの中心 (x,y,z)=(0,0,h) における磁束密度の大きさと向きを求めよ.
- (4)  $I=I_0\sin\omega t$  のとき,円形コイルの誘導電圧 V を求めよ.ここで, $I_0$  は定数, $\omega(\neq 0)$  は 角周波数,t は時間である.円形コイル内の磁束密度は一様とみなせるものとし,その中心 (x,y,z)=(0,0,h) における値を用いて近似してよい.円形コイルを貫く磁束の計算において,微小の隙間は無視してよい.

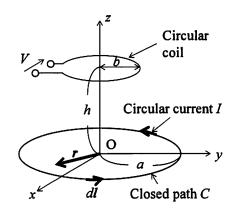


Fig. 1

#### 2022年 2·3月実施 問題1 電磁気学 (2頁目/2頁中)

As shown in Fig. 1, a circular coil made of a lossless conductor is located above a circular current I. The circular current I and the circular coil are parallel to the xy-plane and their radii are a and b, respectively. The center of the circular current I and the circular coil is (x,y,z)=(0,0,0) and (x,y,z)=(0,0,h), respectively. The number of turns of the circular coil is 1. An infinitesimal gap is on the circular coil and an induced voltage V is excited. The circular current I flows along a closed path, C. A line element vector on C is dl. The directions of the circular current I and the line element vector dl are shown in Fig. 1. The circular current I and the circular coil are in vacuum. The position vector is r. The permeability of vacuum is  $\mu_0$ . Answer the following questions.

- (1) Show Faraday's law of electromagnetic induction and give its physical meaning.
- (2) The magnetic dipole moment m of the circular current I is defined as follows. Find m.

$$m{m} = rac{\mu_0 I}{2} \oint_C m{r} imes dm{l}$$

- (3) Find the magnitude and direction of the magnetic flux density at the center of the circular coil (x, y, z) = (0, 0, h).
- (4) Find the induced voltage V of the circular coil when  $I = I_0 \sin \omega t$ . Here,  $I_0$  is constant,  $\omega(\neq 0)$  is the angular frequency, and t is the time. The magnetic flux density inside the circular coil is assumed to be uniform and can be approximated using the value at the center (x, y, z) = (0, 0, h). During calculation of magnetic flux penetrating the circular coil, the infinitesimal gap can be neglected.

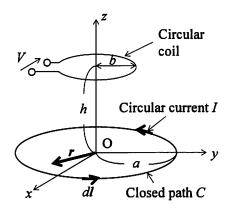


Fig. 1

#### 2022 年 2 · 3 月実施 問題 2 電気回路 (1 頁目/2 頁中)

Fig. 2 に示す回路について、以下の間に答えよ。交流電源の電圧は E [V]、電源の角周波数は  $\omega$  [rad/s]、抵抗は  $R_1$ ,  $R_2$  [ $\Omega$ ]、自己インダクタンスは  $L_1$ ,  $L_2$  [H]、相互インダクタンスは M [H]、インピーダンス素子は Z [ $\Omega$ ] である。また、端子 c-d 間の電圧は  $V_2$  [V] であり、1 次回路側、2 次回路側を流れる電流をそれぞれ  $I_1$ ,  $I_2$  [A] とする.

- (1) T 形等価回路を示せ.
- (2) 2 次回路側の端子 c-d 間を短絡したとき、電流  $I_1$  に対する電流  $I_2$  の電流比  $|I_2|/|I_1|$  を  $\omega, L_2, M, R_2$ で表わせ、また、 $\omega=0$  [rad/s] のときの  $|I_2|/|I_1|$  の値を求めよ.
- (3) 2 次回路側の端子 c-d 間について、Z を取り除いて開放したとき、電源電圧 E に対する 開 放 電 圧  $V_2$  の 電 圧 比  $|V_2|/|E|$  を 求 め よ . た だ し ,  $R_1=10$  [ $\Omega$ ],  $R_2=5$  [ $\Omega$ ],  $L_1=10$  [ $\Omega$ H],  $L_2=5$  [ $\Omega$ H],  $L_3=5$  [ $\Omega$ H],  $L_4=5$  [ $\Omega$ H],  $L_5=5$  [ $\Omega$ H],  $\Omega$ H]
- (4) 端子 a-b 間から見た入力インピーダンス $Z_{ab} = E/I_1 \ \delta \omega, L_1, L_2, M, R_1, R_2, Z$  で表わせ.
- (5) 2 次回路側のZ が理想的なキャパシタC [F] であり、1 次回路側の交流電源の角周波数が  $\omega_0=1/\sqrt{L_2C}$  [rad/s] であるとき、 $Z_{ab}$ を $\omega_0$ ,  $L_1$ , M,  $R_1$ ,  $R_2$ で表わせ、ならびに、 $I_1$  と $I_2$  の位相差が  $\pi/2$  [rad] であることを導け.

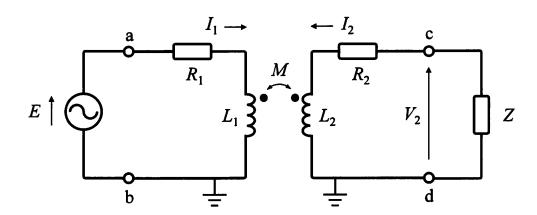


Fig. 2

#### 2022 年 2 · 3 月実施 問題 2 電気回路 (2 頁目/2 頁中)

Answer the following questions regarding the circuit shown in Fig. 2. Here, the voltage of the power source is E[V], the angular frequency of the power source is  $\omega$  [rad/s], the resistances are  $R_1, R_2[\Omega]$ , the self inductances are  $L_1, L_2[H]$ , the mutual inductance is M[H], and the impedance element is  $Z[\Omega]$ . The voltage between points c and d is  $V_2[V]$  and the electric currents on the primary and secondary sides are  $I_1, I_2[A]$ , respectively.

- (1) Show the T-type equivalent circuit.
- (2) In the case that the points c and d are shorted on the secondary side, express the electric current ratio of the electric current on the secondary side  $I_2$  to the electric current on the primary side  $I_1$ ,  $|I_2|/|I_1|$ , by using  $\omega, L_2, M$ , and  $R_2$ . And calculate the value of  $|I_2|/|I_1|$  when  $\omega = 0$  [rad/s].
- (3) In the case that Z is removed and the points c and d are open on the secondary side, calculate the voltage ratio of the open circuit voltage  $V_2$  to the voltage of the power source E,  $|V_2|/|E|$ . Here,  $R_1 = 10 [\Omega]$ ,  $R_2 = 5 [\Omega]$ ,  $L_1 = 10 [\text{mH}]$ ,  $L_2 = 5 [\text{mH}]$ , M = 5 [mH], and  $\omega = 1000 [\text{rad/s}]$ .
- (4) Express the input impedance  $Z_{ab} = E/I_1$  between points a and b by using  $\omega, L_1, L_2, M, R_1, R_2$ , and Z.
- (5) In the case that Z is the ideal capacitance C [F] on the secondary side and the angular frequency of the power source on the primary side is  $\omega_0 = 1/\sqrt{L_2C}$  [rad/s], express  $Z_{ab}$  by using  $\omega_0, L_1, M, R_1$ , and  $R_2$ . In addition, show that the phase difference between  $I_1$  and  $I_2$  is equal to  $\pi/2$  [rad].

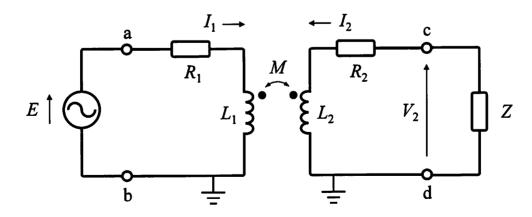


Fig. 2

### 2022年2·3月実施 問題3 情報基礎1 (1頁目/4頁中)


7つのセグメント A,B,C,D,E,F,G から構成される, Fig. 3(a) のような LED 表示器を考える. ただし, どのような入力に対しても, セグメント G は常時白であり, セグメント F は常時黒である.

この表示機は、7種類の 3 ビットの入力 (x,y,z)=(0,0,0), (0,0,1), (0,1,0), (0,1,1), (1,0,0), (1,0,1), (1,1,0) に対して Fig. 3(b) のような出力をそれぞれ与える.このとき,入力 (x,y,z) に対してセグメント  $i\in\{A,B,C,D,E\}$  が黒の場合は 1,白の場合は 0 を出力する論理関数を  $f_i(x,y,z)$  とする.ただし,入力 (x,y,z)=(1,1,1) はドントケア項,すなわち,どのような出力を与えても良い.

以下の問に答えよ.

- (1) 5 つの論理関数  $f_i(x,y,z), i \in \{A,B,C,D,E\}$  の真理値表を記述せよ.
- (2) 論理関数  $f_B(x,y,z)$  の積和最簡形の論理式と和積標準形の論理式を求めよ. 同様に, 論理 関数  $f_E(x,y,z)$  の積和最簡形の論理式と和積標準形の論理式を求めよ.
- (3) 入力 (x,y,z) に対して出力  $(f_B(x,y,z),f_E(x,y,z))$  を与える 3 入力 2 出力論理回路を、2 入力 **AND**、2 入力 **OR**、**NOT** の 3 種類の論理素子のみを用いて構成せよ。ただし、論理素子は Fig. 3(c) のように表記し、回路に使用する素子数はできる限り少なくすること。
- (4) 入力 (x,y,z) に対して出力  $f_B(x,y,z)$  を与える 3 入力 1 出力論理回路を, 3 入力 1 NOR の 論理素子のみを用いて構成せよ。ただし、論理素子は Fig. 3(c) のように表記し、回路に使用する素子数はできる限り少なくすること。

## 2022年2·3月実施 問題3 情報基礎1 (2頁目/4頁中)

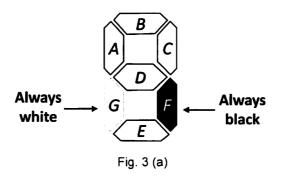

INPUT (x,y,z): (0,0,0) (0,0,1) (0,1,0) (0,1,1) (1,0,0) (1,0,1) (1,1,0)

Fig. 3 (b)

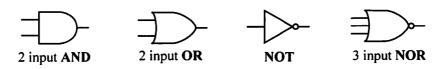


Fig. 3 (c)

### 2022年2·3月実施 問題3 情報基礎1 (3頁目/4頁中)


Consider the LED display shown in Fig. 3(a), which consists of 7 segments A, B, C, D, E, F, G. Here, for any input, the segment G is always white, and the segment F is always black.

The display gives outputs as shown in Fig. 3(b) according to 7 kinds of 3-bit inputs (x,y,z)=(0,0,0), (0,0,1), (0,1,0), (0,1,1), (1,0,0), (1,0,1), and (1,1,0), respectively. Let  $f_i(x,y,z)$  be a logical function that outputs 1 if segment  $i \in \{A,B,C,D,E\}$  is black and 0 if it is white for input (x,y,z). Here, the input (x,y,z)=(1,1,1) is a "don't care term," i.e., it can give any output.

Answer the following questions.

- (1) Show the truth table for the five logical functions  $f_i(x, y, z), i \in \{A, B, C, D, E\}$ .
- (2) Show the logical expression of the logic function  $f_B(x, y, z)$  in the minimum sum of products form and in the canonical product of sum form. Similarly, show the logical expression of the logic function  $f_E(x, y, z)$  in the minimum sum of products form and in the canonical product of sum form.
- (3) Construct a 3-input 2-output logic circuit that gives output  $(f_B(x, y, z), f_E(x, y, z))$  for input (x, y, z) using only 3 kinds of the logic elements: 2-input **AND**, 2-input **OR**, and **NOT**. Here, the logic elements should be represented as shown in Fig. 3(c), and the number of logic elements used in the circuit should be as small as possible.
- (4) Construct a 3-input 1-output logic circuit that gives output  $f_B(x, y, z)$  for input (x, y, z) using only the 3-input **NOR** logic elements. Here, the 3-input **NOR** logic element should be represented as shown in Fig. 3(c), and the number of logic elements used in the circuit should be as small as possible.

## 2022年2·3月実施 問題3 情報基礎1 (4頁目/4頁中)

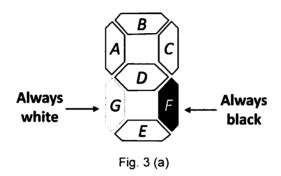

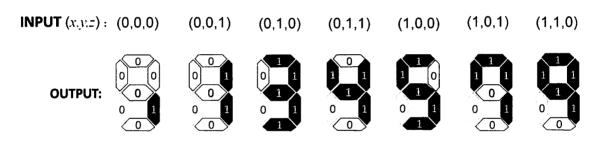


Fig. 3 (b)

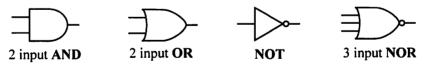


Fig. 3 (c)

#### 2022年 2·3月実施 問題4情報基礎2 (1頁目/2頁中)

#### 以下の問に答えよ.

- (1) m を正の整数とおく、2m 個の互いに異なる値がある、そのうち m 個の値が配列  $A_1$  に昇順 に格納されている、残りの m 個の値が配列  $A_2$  に昇順に格納されている、
  - $A_1$  と  $A_2$  から値を取り出して,すべての値が昇順になるように配列 B に格納する手順を考える.最悪時間計算量が O(m) であるような手順を簡潔に示せ.
- (2) n 個の互いに異なる値が格納された配列 C を考える。ただし, $n=2^p$  であり, p は正の整数である。幾つかの変数と配列 C に加えて,長さが n の配列を一つだけ作業領域として使用してよい。
  - (a) 問 (1) の手順を用いて、配列 C に格納された値を昇順に整列することを考える. 最悪時間計算量が  $O(n \log n)$  であるような整列手順を、簡潔に説明せよ.
  - (b) (a) の手順の最悪時間計算量が $O(n \log n)$ となる理由を,簡潔に説明せよ.
- (3) k を正の整数とおく. ある広い定義域の中で, k 個の互いに異なる値を考える. これらの値が配列に格納されているものとする.

これらの値がある条件を満たしているとき,基数ソートを用いることで,値の初期の順序に依らず,値を線形時間 O(k) で整列することができる.時間計算量が O(k) となるような条件を一つ示せ.

#### 2022年 2·3月実施 問題4情報基礎2 (2頁目/2頁中)


#### Answer the following questions.

- (1) Let m be a positive integer. There exist 2m values which are different from each other. m values out of them are stored in an array  $A_1$  in ascending order. The remaining m values are stored in an array  $A_2$  in ascending order.
  - Consider a procedure for taking all the values out of  $A_1$  and  $A_2$ , and storing them in an array B so that all values are in ascending order. Explain briefly the procedure whose worst-case time complexity is O(m).
- (2) Consider an array C holding n values which are different from each other, where  $n = 2^p$  and p is a positive integer. Only one array whose length is n can be used as a working space in addition to some variables and the array C.
  - (a) Consider sorting the values stored in the array C in ascending order using the procedure in question (1).
    - Explain briefly a sorting procedure whose worst-case time complexity is  $O(n \log n)$ .
  - (b) Explain briefly the reason why the worst-case time complexity of the procedure in (a) is  $O(n \log n)$ .
- (3) Let k be a positive integer. Consider k values which are different from each other in a large domain of definition. Suppose these values are stored in an array.
  - When these values satisfy a certain condition, it is possible to sort the values in linear time O(k) by using Radix Sort regardless the initial order of the values. Show a condition in which the time complexity becomes O(k).

#### 2022 年 2 · 3 月実施 問題 5 物理基礎 (1 頁目 / 2 頁中)

Fig. 5 (a)に示すように、質量の無視できる棒が、長さ a で質量の無視できる 2 本のひもで水平な天井から吊されている. 棒をつり下げている 2 本のひもは平行で、棒は常に水平である. 棒の両端には、質量 m の質点 A および B が、長さが l で質量の無視できるひもでそれぞれつり下げられている. Fig. 5 (b)に示すように、棒および質点が xy 面内で運動する場合について考える. 棒をつり下げているひもが鉛直下向き方向(-y方向)となす角度を $\theta$ 、質点 A および B が-y方向となす揺れ角度をそれぞれ  $\varphi_1$  および  $\varphi_2$  とし、 $\varphi=\varphi_1-\varphi_2$  とおく. また、質点 A および B の水平方向(x 方向)の変位をそれぞれ  $x_1$  および  $x_2$ 、重力加速度(x  $x_2$  の大きさを $x_3$   $x_4$   $x_5$   $x_5$   $x_5$   $x_6$   $x_6$   $x_6$   $x_6$   $x_7$   $x_8$   $x_7$   $x_8$   $x_8$  x

- (1) 質点 A および B の運動方程式を求めよ.
- (2) 棒の質量が無視できるとき、棒の両端にかかる力は釣り合う。この時、 $\theta$ と $\varphi_1$ および $\varphi_2$ との関係を求めよ。
- (3) この系の基準座標を $\varphi = \varphi_1 \varphi_2$  および  $\theta$  とする.  $\varphi$  および  $\theta$  それぞれに対する基準角振動数(固有角振動数) $\omega_{\varphi}$  および  $\omega_{\theta}$  を求めよ. また,  $\omega_{\varphi}$  および  $\omega_{\theta}$  の大小関係を示し, その理由を定性的に論ぜよ.
- (4)  $\theta=0$ とした場合、および $\varphi=0$ とした場合のそれぞれについて、 $\theta$ ,  $\varphi_1$ ,  $\varphi_2$  の時間変化の概略をグラフに表せ.

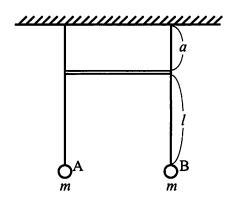

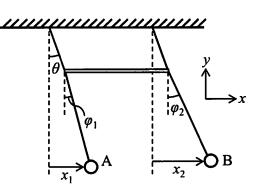


Fig. 5 (a)

Fig. 5 (b)

#### 2022 年 2 · 3 月実施 問題 5 物理基礎 (2頁目/2頁中)

As shown in Fig. 5 (a), a rod of negligible mass is suspended from a horizontal ceiling by two strings of length a and negligible mass. The two strings suspending the rod are assumed to be parallel and the rod is always horizontal. At each end of the rod, the mass points A and B of mass m are suspended by a string of length l and negligible mass, respectively. As shown in Fig. 5 (b), consider the case where the rod is moving in the xy-plane. Let the angle of the string suspending the rod with respect to the vertical downward direction (-y direction) be  $\theta$ , the swing angle of the mass points A and B with respect to the -y direction be  $\varphi_1$  and  $\varphi_2$ , respectively, and  $\varphi = \varphi_1 - \varphi_2$ . Also, let the displacements of the mass points A and B in the horizontal direction (x direction) be  $x_1$  and  $x_2$ , respectively, and the magnitude of the gravitational acceleration (-y direction) be g. Here, g is assumed to be small and can be approximated as  $\sin \theta \simeq \theta$  and  $\cos \theta \simeq 1$ .  $\varphi_1$  and  $\varphi_2$  are also assumed to be small and can be approximated in the same way. Answer the following questions.

- (1) Find the equations of motion for the mass points A and B.
- (2) When the mass of the rod is negligible, the forces acting on both ends of the rod are balanced. Find the relationship among  $\theta$ ,  $\varphi_1$  and  $\varphi_2$ .
- (3) The reference coordinates of this system are  $\varphi = \varphi_1 \varphi_2$  and  $\theta$ . Find the reference angular frequencies (natural angular frequencies)  $\omega_{\varphi}$  and  $\omega_{\theta}$  for  $\varphi$  and  $\theta$ , respectively. Obtain the relationship between the magnitudes of  $\omega_{\varphi}$  and  $\omega_{\theta}$ , and discuss the reasons qualitatively.
- (4) For the two cases of  $\theta = 0$  and  $\varphi = 0$ , sketch the dynamics of  $\theta$ ,  $\varphi_1$  and  $\varphi_2$  on a graph.

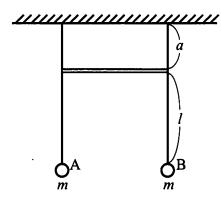


Fig. 5 (a)

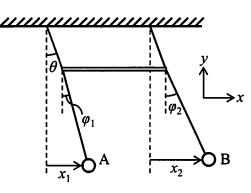


Fig. 5 (b)

#### Question No. 6: Basic mathematics (1/2)

#### 2022 年 2 • 3 月実施 問題 6 数学基礎 (1 頁目/2 頁中)

(1) 行列
$$A = \begin{pmatrix} 1 & 2 & 0 \\ -1 & -2 & 1 \\ 0 & 0 & 1 \end{pmatrix}$$
 について考える. 以下の問に答えよ.

- (a) Aのすべての固有値と、それに対応する固有ベクトルを求めよ、
- (b) 行列に関する方程式,  $A^3 + aA^2 + bA + cE = O$  の係数 a, b, c を求めよ. ただし, E は 3 行 3 列の単位行列, O は零行列である.
- (c) 行列  $A^4 + A^3 A^2 + 4A 5E$  を計算せよ.
- (2) 関数f(t)のラプラス変換を $F(s) = \mathcal{L}[f(t)] = \int_0^\infty e^{-st} f(t) dt$  とする. 以下の問に答えよ.

$$(a)\mathscr{L}[f(at+b)] = \frac{e^{bs/a}}{a} \left\{ F\left(\frac{s}{a}\right) - \int_0^b e^{-st/a} f(t) dt \right\}$$
となることを導け、ここで、 $a > 0$ . また、
$$at + b \le 0$$
 のとき、 $f(at+b) = 0$  である.

(b) 上式を用いて, 以下の差分方程式,

$$\begin{cases} f(t+2)-3f(t+1)+2f(t)=t & (t \ge 0) \\ f(t)=0 & (0 \le t \le 2), \end{cases}$$

を満たすf(t)に対するF(s)を求めよ.

#### Question No. 6: Basic mathematics (2/2)

#### 2022 年 2 · 3 月実施 問題 6 数学基礎 (2 頁目/2 頁中)

- (1) Consider the matrix  $A = \begin{pmatrix} 1 & 2 & 0 \\ -1 & -2 & 1 \\ 0 & 0 & 1 \end{pmatrix}$ . Answer the following questions.
  - (a) Find all the eigenvalues and the corresponding eigenvectors of A.
  - (b) Find coefficients a, b, and c for a matricial equation  $A^3 + aA^2 + bA + cE = O$ . Here, E is the  $3 \times 3$  unit matrix and O is the zero matrix.
  - (c) Calculate the matrix of  $A^4 + A^3 A^2 + 4A 5E$ .

Answer the following questions.

- (2) Let  $F(s) = \mathcal{L}[f(t)] \equiv \int_0^\infty e^{-st} f(t) dt$  be the Laplace transform of the function f(t).
  - (a) Show that  $\mathscr{L}[f(at+b)] = \frac{e^{bs/a}}{a} \left\{ F\left(\frac{s}{a}\right) \int_0^b e^{-st/a} f(t) dt \right\}.$ Here, a > 0. Also f(at+b) = 0, where  $at + b \le 0$ .
  - (b) By using the above formula, find F(s) of f(t) satisfying the following difference equation,

$$\begin{cases} f(t+2)-3f(t+1)+2f(t)=t & (t \ge 0) \\ f(t)=0 & (0 \le t \le 2). \end{cases}$$